

HW #3 ENGR 065 - 2

2. a) Compute equivalent resistance seen by the independent current source

$2R'$, " \bar{Z} " in parallel

$$2R \parallel 2R = \frac{2R \cdot 2R}{2R+2R} = \frac{4R^2}{4R} = R$$

Now $R+R=2R$
and $2R \parallel 2R = \frac{R \cdot 2R}{R+2R} = \frac{2R^2}{3R} = \boxed{\frac{2}{3}R = R_{eq}}$

- b) The equivalent resistance of the following circuit is $R_{eq}=50\Omega$
Find R

$$R_{eq}=50\Omega$$

$$\frac{1}{R_1} = \frac{1}{12} \Rightarrow R_1 = 12\Omega$$

$$R_2 = 10 + R + 4$$

$$\frac{1}{R_1} = \frac{1}{12} + \frac{1}{12} + \frac{1}{12} = \frac{3}{12} = \frac{1}{4}$$

$$R_2 = (14 + R)\Omega$$

$$R_{eq} = 30 + (60 \parallel 14 + R)$$

$$50 = 30 + (60 \parallel 14 + R)$$

$$\boxed{R = 16\Omega}$$

$$20 = \frac{60 \cdot (14 + R)}{16(14 + R)}$$

$$\frac{1}{3} = \frac{14 + R}{74 + R} \Rightarrow 74 + R = 3(14 + R) \Rightarrow 74 + R = 42 + 3R$$

$$32 = 24$$