

## HW#1 ENGR 065

#3 b) Find the total energy delivered by the element.

$$\begin{aligned}
 E &= \int_0^{\infty} P(t) dt = \int_0^{\infty} 3/5 e^{-500t} dt \\
 &= \frac{3}{5} \left( \frac{e^{-500t}}{-500} \right) \Big|_0^{\infty} = \frac{-3}{5(500)} \left( e^{-500(\infty)} - e^{-500(0)} \right) \\
 &= \frac{-3}{5(500)} (0 - 1) \quad \begin{matrix} \lim_{t \rightarrow \infty} e^{-500(\infty)} \\ - \lim_{t \rightarrow 0} e^{-500t} - 0 \end{matrix} \\
 &= \frac{-3}{5(500)} (-1) \Rightarrow \frac{3}{5(500)} = \frac{3}{2500} \Rightarrow \frac{3}{2.5 \cdot 10^3} \\
 E &= 1.2 \cdot 10^{-3} J \Rightarrow \boxed{1.2 \text{ mJ}}
 \end{aligned}$$

#4	<u>Element</u>	<u>Voltage(V)</u>	<u>Current(mA)</u>	<u>D/A</u>
a	-3	-250	Delivering	
b	4	-400	Absorbing	
c	1	400	Delivering	
d	1	150	Absorbing	
e	-4	200	Delivering	
f	4	50	Absorbing	

$$P_{\text{delivering}} = P_{\text{Absorbing}} \Rightarrow P_a + P_c + P_e = P_b + P_d + P_f$$

$$\begin{aligned}
 &= (3 \cdot 250 \cdot 10^{-3}) + (1 \cdot 400 \cdot 10^{-3}) + (4 \cdot 200 \cdot 10^{-3}) = (4 \cdot 400 \cdot 10^{-3}) + (1 \cdot 150 \cdot 10^{-3}) \\
 &\quad + (4 \cdot 50 \cdot 10^{-3})
 \end{aligned}$$

$$\boxed{1.95 = 1.95}$$

watts