

# ENGR 065: HW #4

$$\begin{aligned} R_2 &= 100\text{k}\Omega \\ R_m &= 100\text{k}\Omega \\ R_S &= 10\text{k}\Omega \\ R_1 &= 20\text{k}\Omega \end{aligned}$$

$$\begin{aligned} R_2 &= 100\text{k}\Omega \\ R_S &= 10\text{k}\Omega \\ R_1 &= 20\text{k}\Omega \end{aligned}$$

$$V_o = (40) \left( \frac{100k}{10k+20k+100k} \right)$$

$$= (40) \left( \frac{100k}{130k} \right) = 30.769\text{V}$$


$$V_o = (V_s) \left[ \frac{(R_2 \parallel R_m)}{R_S + R_1 + (R_2 \parallel R_m)} \right]$$

$$V_o = (40) \left[ \frac{(100k \parallel 100k)}{10k + 20k + (1k \parallel 100k)} \right]$$

$$= (40) \left[ \frac{(100k)(100k)}{100k + 100k} \right] \Rightarrow (40) \left( \frac{50k}{30k + 50k} \right)$$

$$\begin{aligned} &= 40 \left( \frac{50}{80} \right) \\ &= 25\text{V} \end{aligned}$$

2. a)

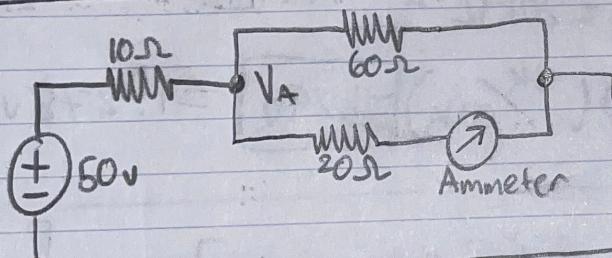


ideally it has Ø internal resistance

$$\frac{V_A - 50}{10} + \frac{V_A}{60} + \frac{V_A}{20} = 0$$

$$6V_A - 300 + V_A + 3V_A = 0$$

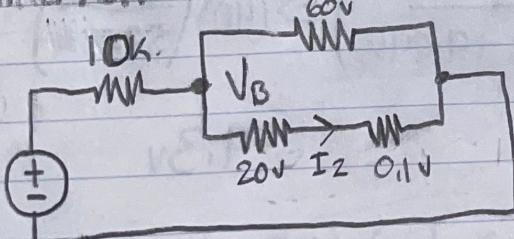b) Using a real ammeter with an internal resistance 0.1Ω



$$10V_A - 300 = 0$$

$$V_A = \frac{300}{10} = 30\text{V}$$

$$V_A = 30\text{V}$$

$$\frac{V_B - 50}{10} + \frac{V_B}{60} + \frac{10V_B}{20} = 0$$

$$\Rightarrow \frac{669V_B}{669} = \frac{20100}{669} = 30.044$$

$$I_2 = \frac{V_B}{20.1} = \frac{30.044}{20.1} = 1.493\text{A}$$